

Lab 02

spice

Contents

Contents	2
Part 1 (prelab).....	3
PART2	5
1 In circuit1 (overdamping):	6
2 In circuit2 (critical):	8
3 In circuit3 (underdamping):	10
PART3	12
BOUNS	14

Part 1 (prelab)

CODE IN PART1 FOLDER


```
1 % cleaning the workspace, and cmd window
2 - clear all;
3 - clc;
4
5 % running the first SPICE netlist
6 - fprintf('the first netlist:\n');
7 - [sum,num]=Solve_Circuit('circuit_1.cir');
8
9 - clear all; % used to bypass an error only with Octave (not MATLAB)
10 |
11
12 - fprintf('the second netlist:\n');
13 - [sum,num]=Solve_Circuit('circuit_2.cir');
14
15
```

the first netlist:

```
V_1 = 30.000000
V_2 = 16.956522
I_Vb = -0.260870
```

the second netlist:

```
V_1 = 40.000000
V_2 = 14.634146
V_3 = 32.195122
V_4 = 112.195122
I_Vb = -1.268293
```

 Linear Circuit

--- Operating Point ---

V(1):	30	voltage
V(2):	16.9565	voltage
I(Is):	2	device_current
I(R1):	0.26087	device_current
I(R2):	0.565217	device_current
I(R3):	1.69565	device_current
I(Vb):	-0.26087	device_current

```

Linear Circuit
--- Operating Point ---
V(1) :      40      voltage
V(2) :     14.6341   voltage
V(3) :     32.1951   voltage
V(4) :    112.195    voltage
I(Is) :      1      device_current
I(R1) :     1.26829   device_current
I(R2) :    -0.195122   device_current
I(R3) :     -1      device_current
I(R4) :     1.46341   device_current
I(R6) :     0.804878   device_current
I(Vb) :    -1.26829   device_current


```

		LT SPICE	OUR CODE
CIRCUIT1	V(1)	30	30
	V(2)	16.956522	16.9565
	I(VB)	-0.260870	-0.260870
CIRCUIT2	V(1)	40	40
	V(2)	14.6341	14.634146
	V(3)	32.1951	32.195122
	V(4)	112.195	112.195122
	I(VB)	-1.26829	-1.268293

Same results, but LT SPICE counts every current in the circuit, our code only calculate the current in the voltage sources.

PART2

CODE IN PART2 FOLDER

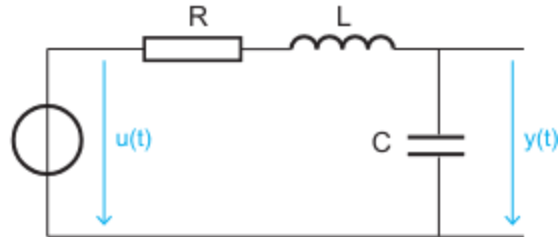

$$\frac{y(t)}{u(t)} = \frac{\frac{1}{sC}}{\frac{1}{sC} + R + LS} = \frac{1}{1 + RCS + LCS^2} = \frac{\frac{1}{LC}}{s^2 + \frac{R}{L}s + \frac{1}{LC}}$$

$$\omega_0^2 = \frac{1}{LC}, \omega_0 = \frac{1}{\sqrt{LC}}$$


$$\frac{\omega_0}{Q} = \frac{R}{L}$$



I added support for inductors, capacitors, and AC analysis, and changed the parsing of the netlist to read the user .ac command and also voltage source type.

1 IN CIRCUIT1 (OVERDAMPING):

$R=3000$, $C=10\text{n}$, $L=10\text{m}$

$\omega_0 = 0.1\text{MHz}$, $Q=0.333$

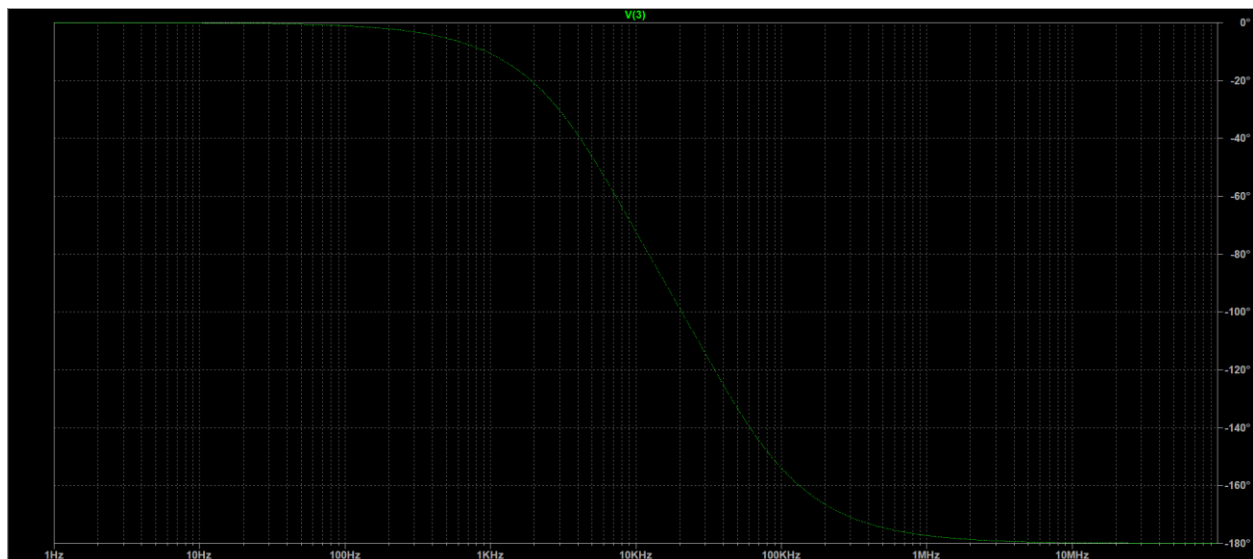


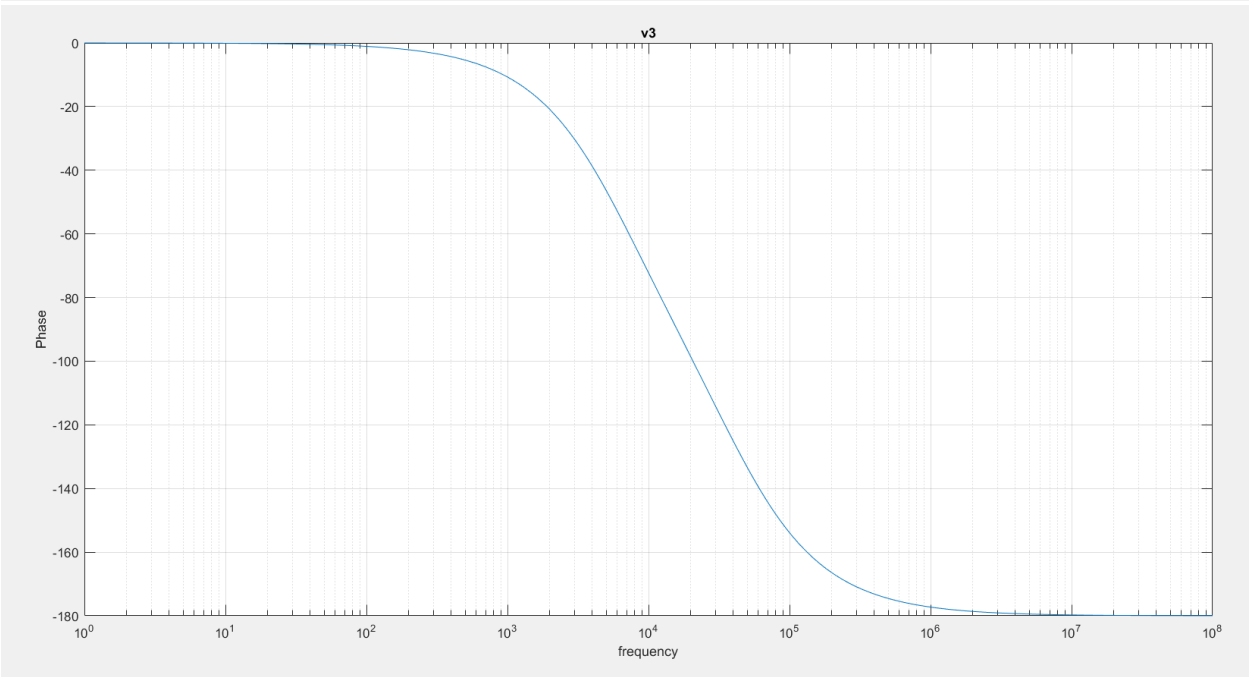
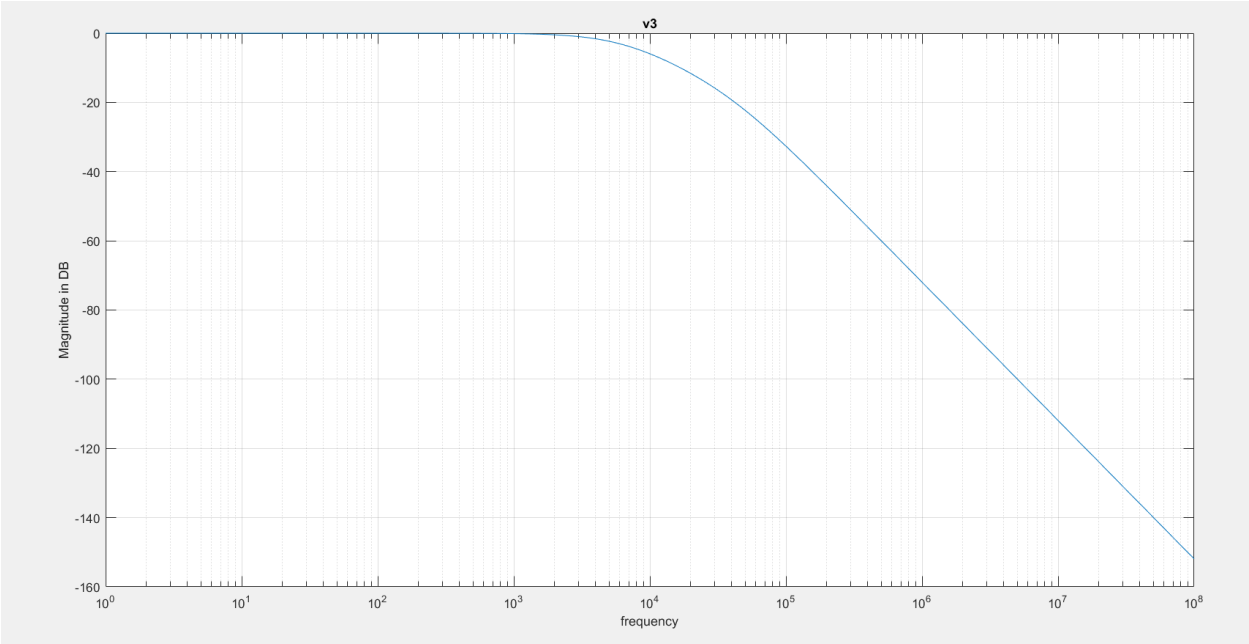


2 IN CIRCUIT2 (CRITICAL):

$R=2000$, $C=10n$, $L=10m$

$\omega_0 = 0.1MHz$, $Q=0.5$

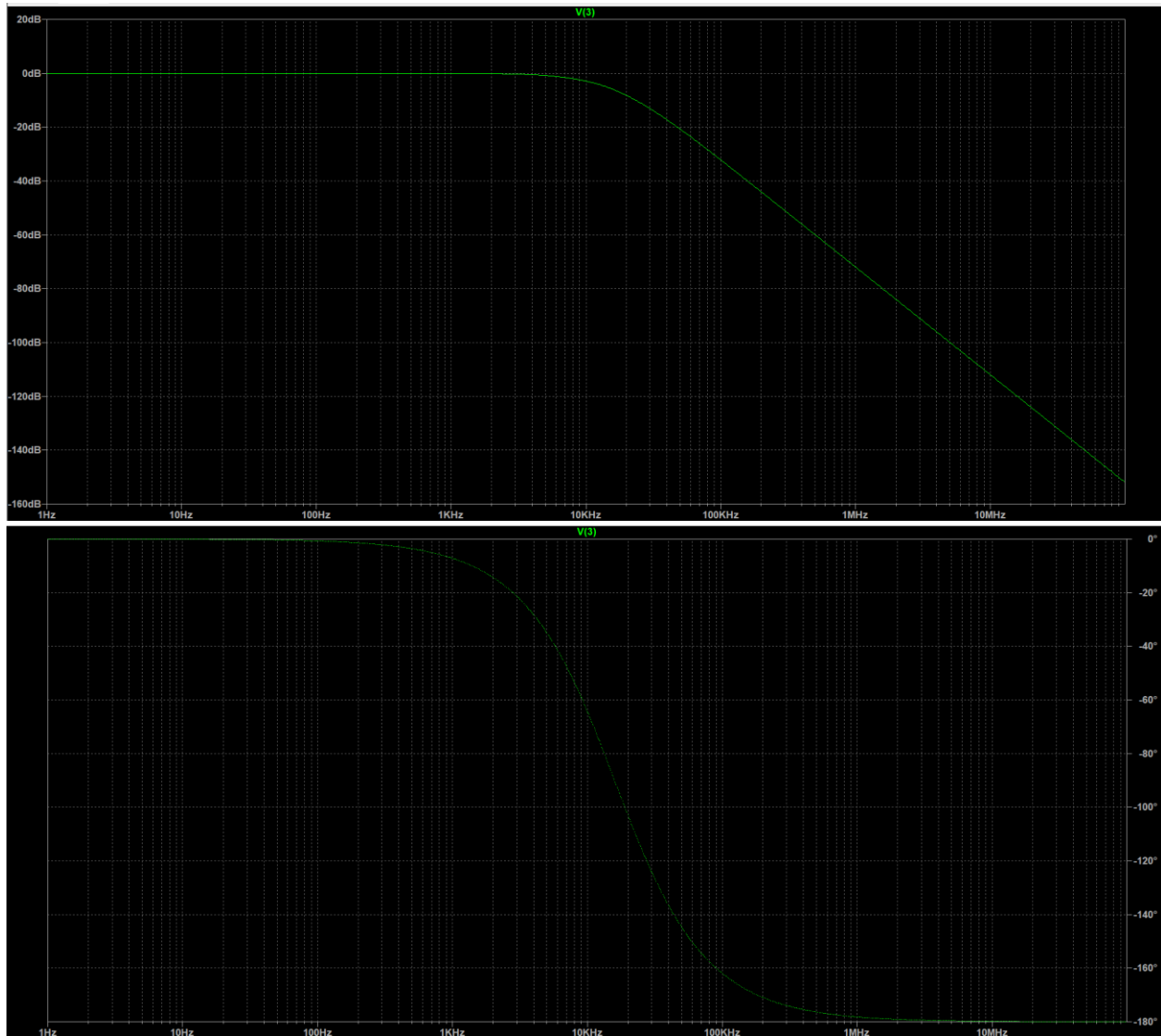


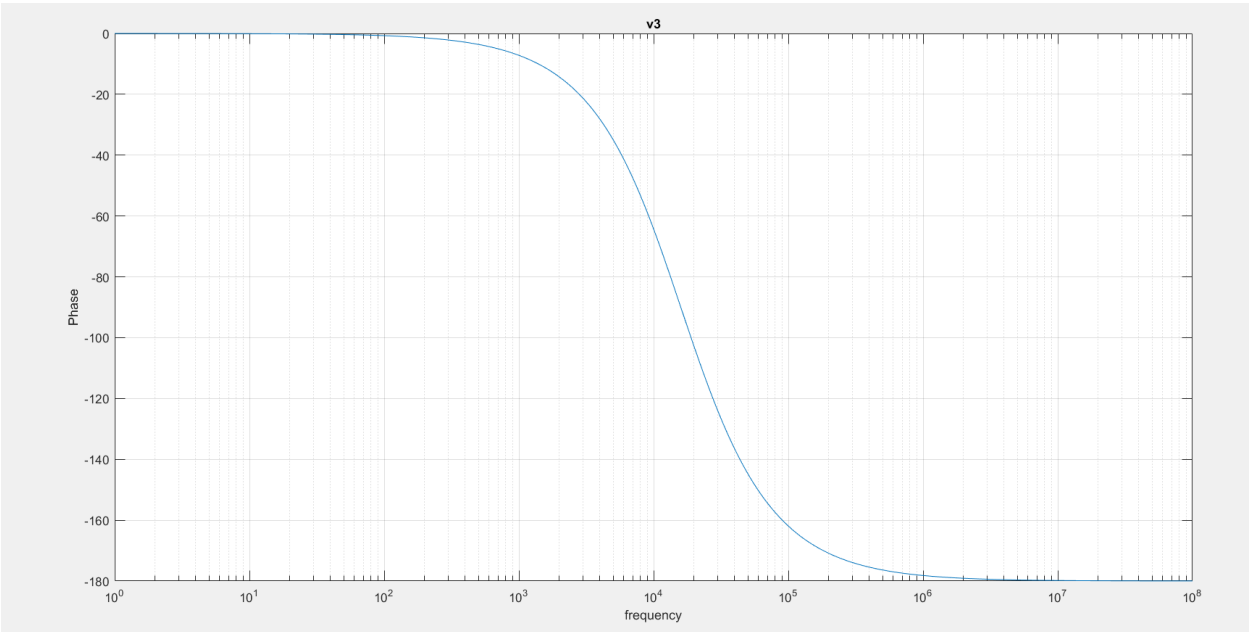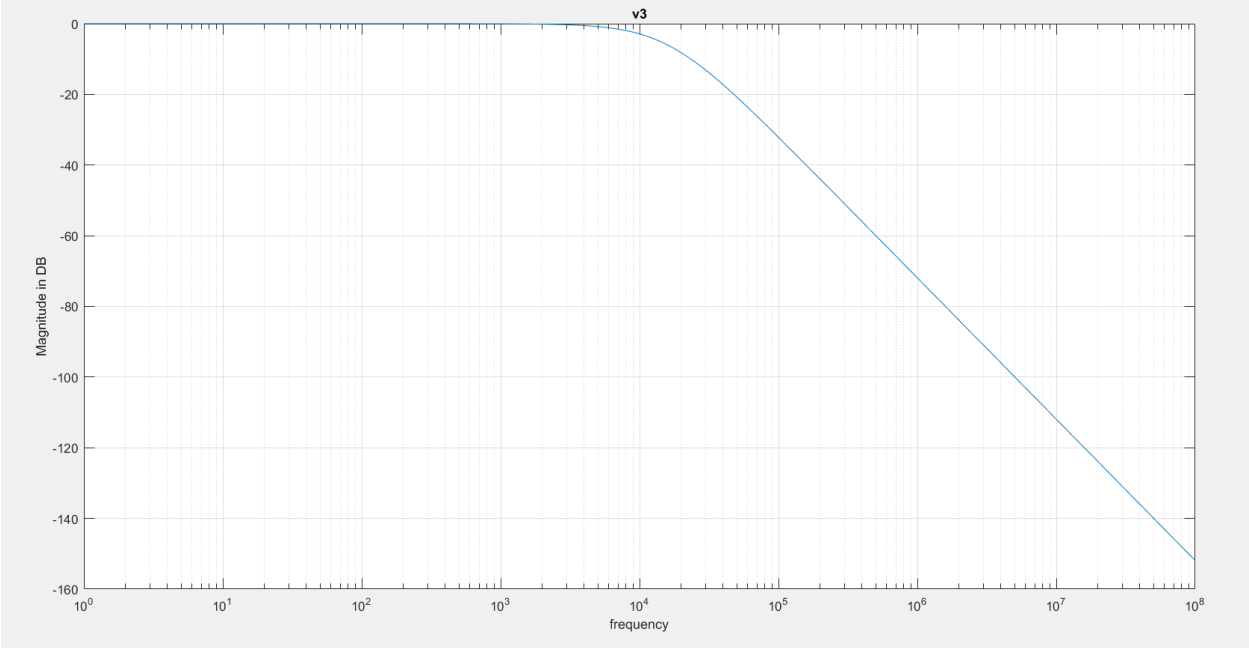


3 IN CIRCUIT3 (UNDERDAMPING):

$R=500$, $C=10\text{n}$, $L=10\text{m}$

$\omega_0 = 0.1\text{MHz}$, $Q=2$

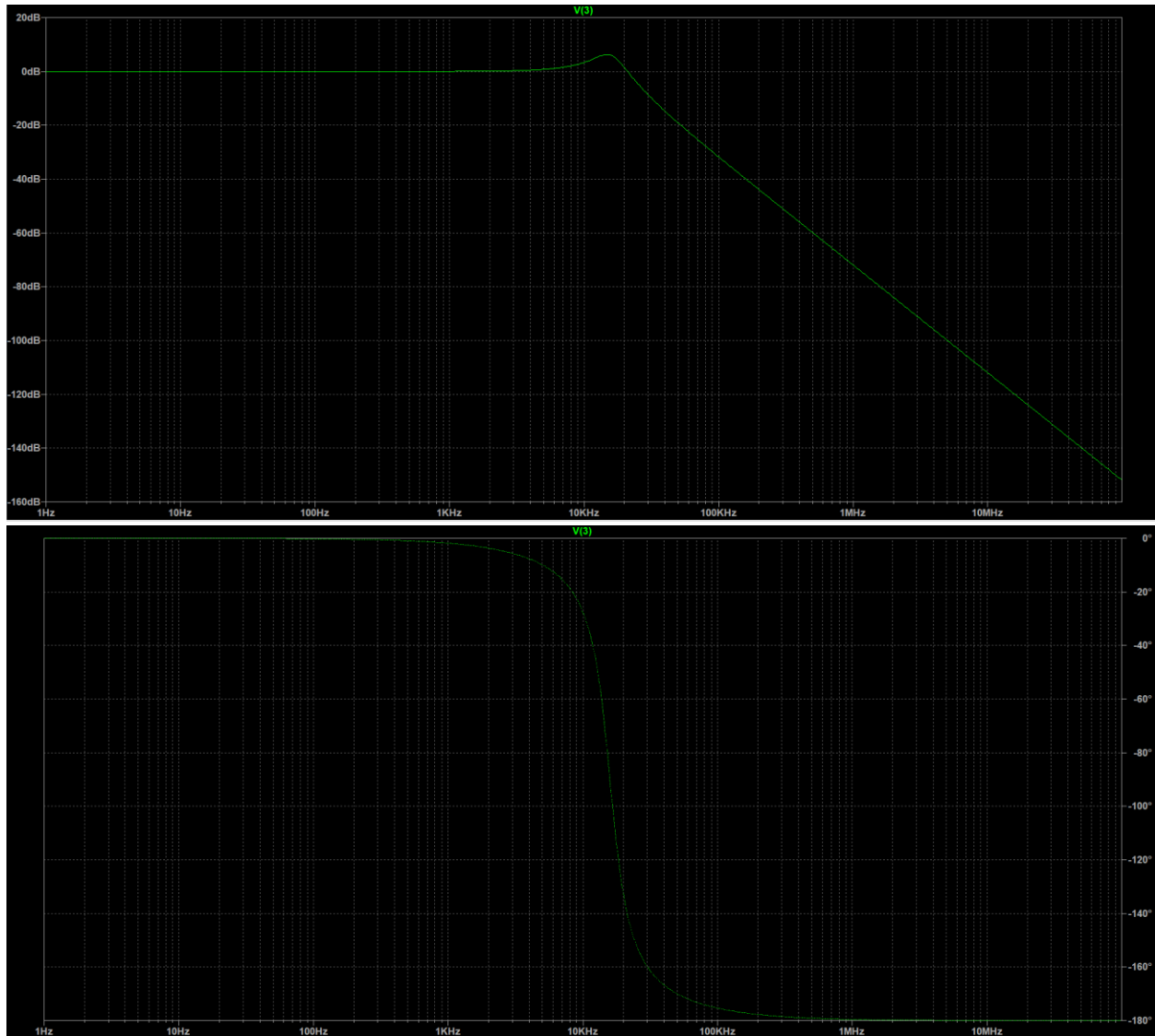

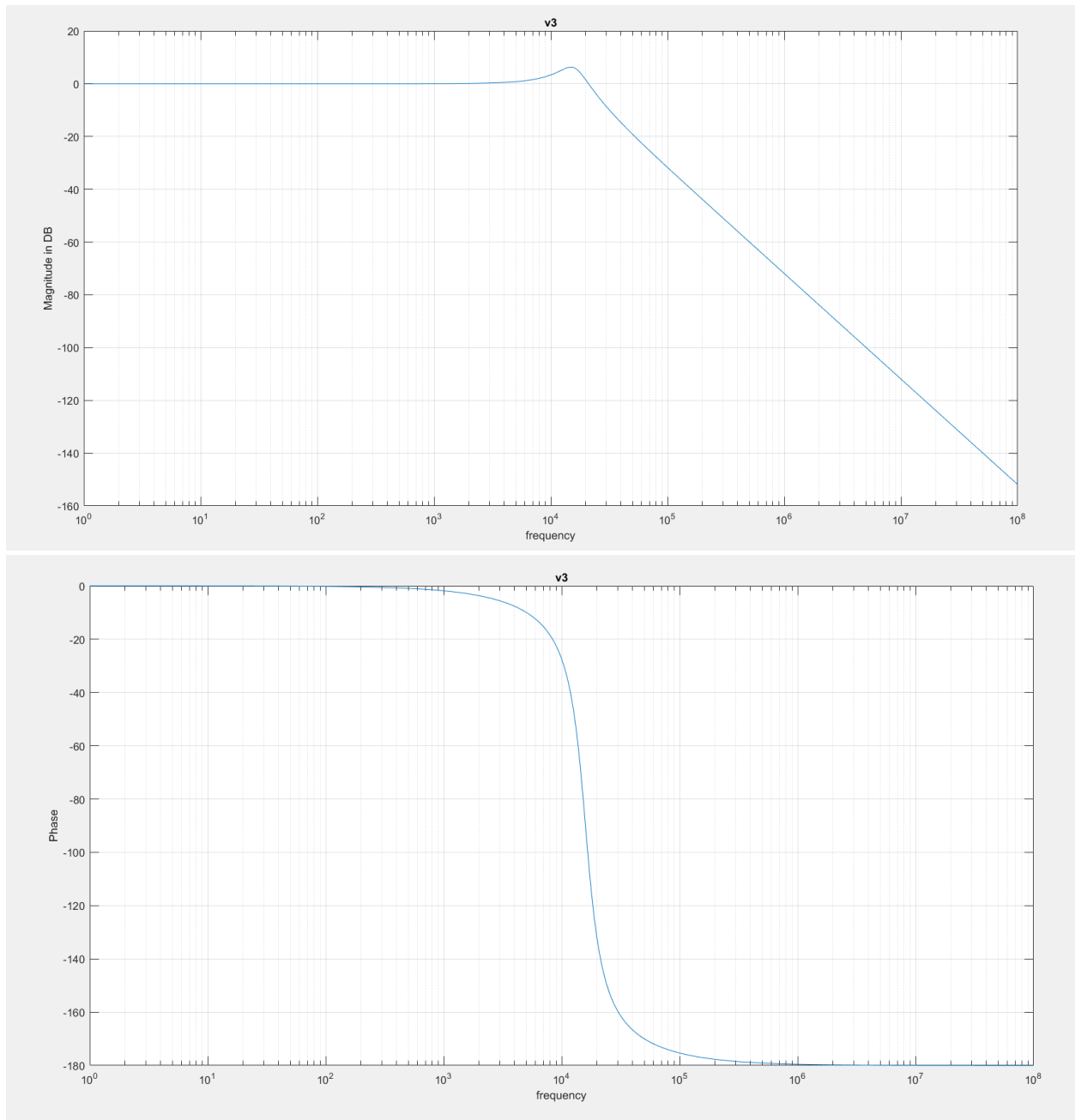



The results are pretty much the same.

the code shows all bode plots for all unknown node's voltages, and currents in voltage sources, like we had in the lecture.

PART3

CODE IN PART3 FOLDER



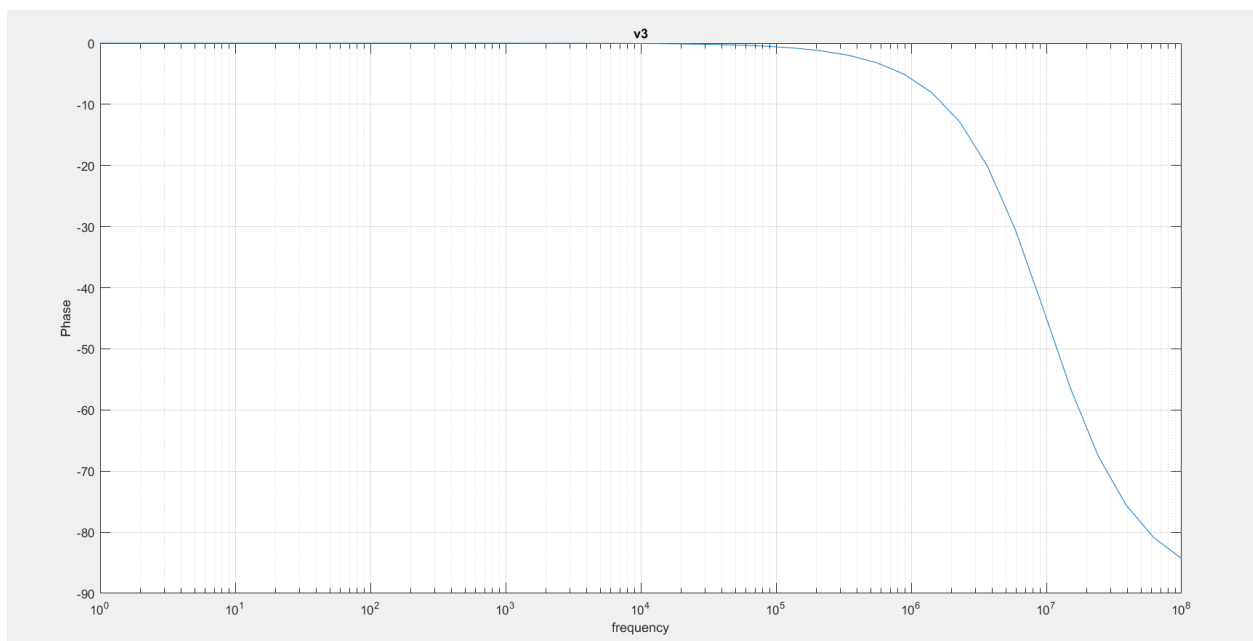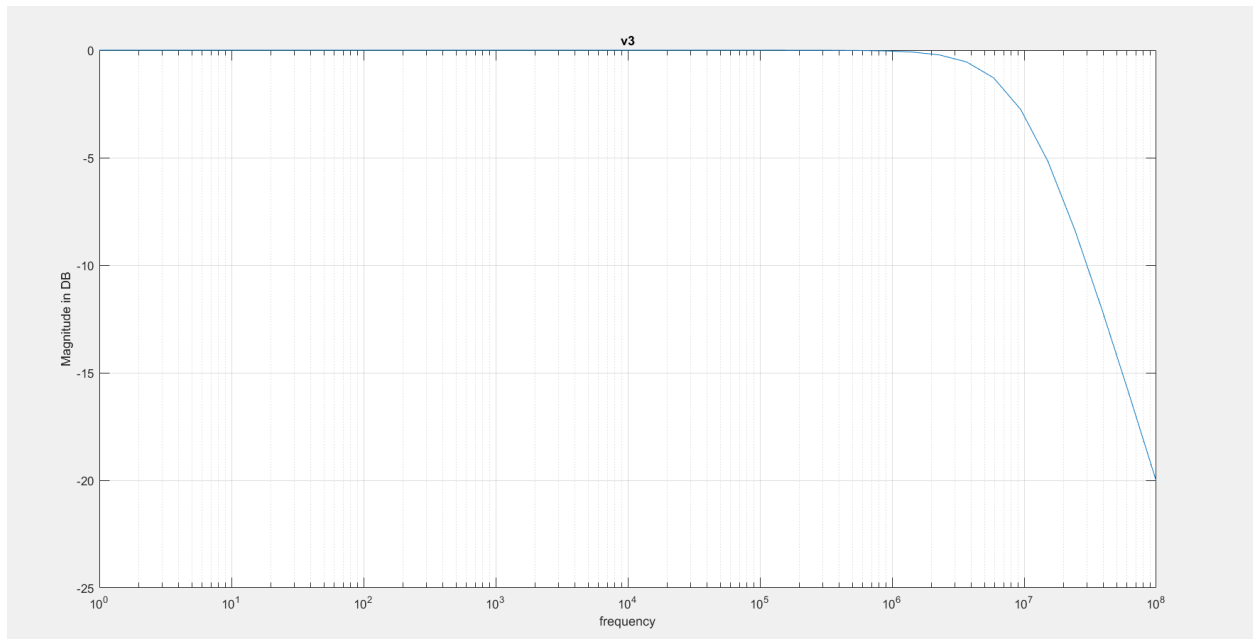

The results are pretty much the same.

BOUNS

```
if instances_key=='.'  
    if strcmp(splitted_line(1),'.AC') || strcmp(splitted_line(1),'.ac')  
        Node_1 = [splitted_line(2)];  
  
        Node_2 = [splitted_line(3)]; %n  
        Node_2=prefixes(Node_2);  
  
        Values = [splitted_line(4)]; %fmin  
        Values=prefixes(Values);  
  
        Names = [splitted_line(5)]; %fmax  
        Names=prefixes(Names);  
  
    continue;  
    end  
    continue;  
end
```

```
[DEC n fmin fmax] = ParseNetlist(netlist, '.');
```

```
fmax=str2double(fmax) ;
```

```
fmin=str2double (fmin) ;
```

```
n=str2double (n) ;
```

```
f=logspace(log10(fmin),log10(fmax),log10(fmax)*n) ;
```

```
] for k=1:length(f)
```

```
    S=1i*2*pi*f(k) ;
```

```
    numeric_ans=subs(symbolic_ans);
```

```
]     for ii = 1:1:numel(symbolic_ans)
```

```
    solv(ii,k)=double(numeric_ans(ii));
```

```
-     end
```

```
-end
```

The frequency isn't manually inserted but it changes with the netlist, also I made Prefixes a function in part3, as we use it a lot in this case (with fmax, fmin)